


Lesson 3:

Parallel Circuits

Draw the Schematic Circuit Diagram for the circuit below.

Circuit Picture

Schematic Diagram

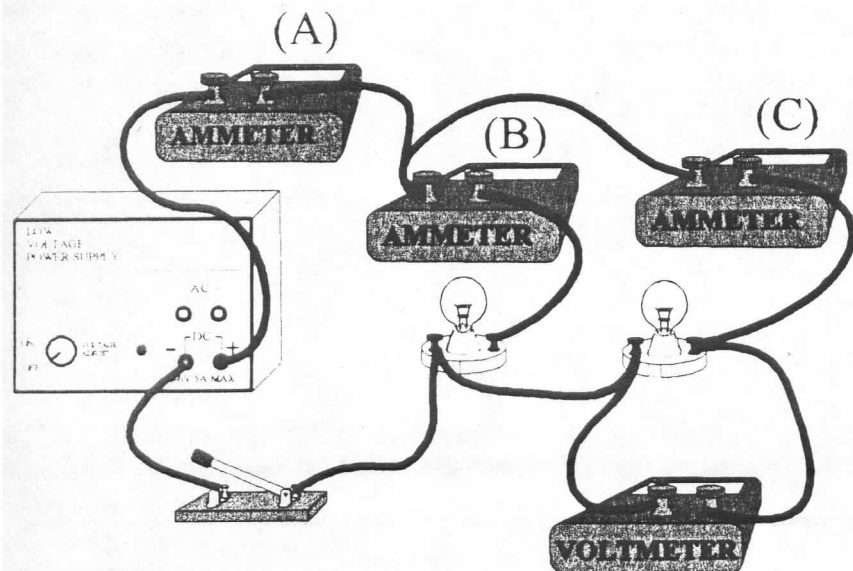

- 2) When bulbs (or anything else) are connected side by side so that the current must divide at branch points, we call it a _____ circuit.
- 3) In the above circuit, if the voltage (potential) gain across the source is 1 Volt, what does our model predict about the voltage drop across the light bulb will be? Explain.
- 4) What does our model predict the voltage drop across the other light bulb will be? Explain.
- 5) If the voltage drop across the light bulbs is the same, what does our model predict the current through the bulbs will be? Explain.
- 6) Assume both bulbs are identical. In the above circuit, if the electric current through Ammeter (C) is one coulomb per second, then the current through Ammeter (B) will be _____ coulomb per second. What does our model predict about the electric current through Ammeter (A)? Explain.

- 7) If more bulbs are connected in parallel, what does our model predict about the brightness of each bulb? Explain
- 8) If more bulbs are connected in parallel, what does our model predict about the current in the main circuit [Ammeter (A)]?
- 9) If more bulbs are connected in parallel, what does our model predict about the current in the branches [Ammeter (B) and Ammeter (C) or any additional ammeter]?
- 10) As more bulbs are connected in parallel, what will happen to the number of paths for the current to flow?
- 11) In a parallel circuit, if one light bulb burns out, what does our model predict will happen to
- A) the current in the main circuit [Ammeter (A)]?
 - B) the current in the branch circuits [Ammeter (B) or (C)]?
 - C) the brightness of the remaining bulbs?
- 12) Is there ever any parallel circuit where one branch gets all the current and the other gets none ?"